

Detroit, Michigan, USA





Eliminating the High Voltage Precharge with Existing Hardware in BEV (24AE-0244)

Patrick Kowalyk


Automotive FAE



- What is a precharge
- Why is it important
- Challenges precharging from a high-voltage source
- Regulation is required
- Comparisons of precharges
- Power flow
- Advantages of using a precharge from a low voltage source


Precharge prevents damage to parts and equipment

In-rush current is high

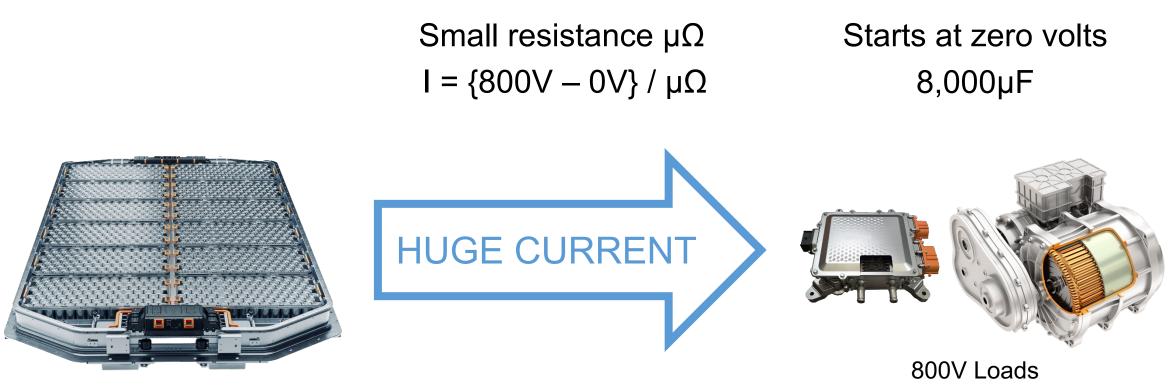

800V Traction Battery

Ringing from dV/dt with loads C and L

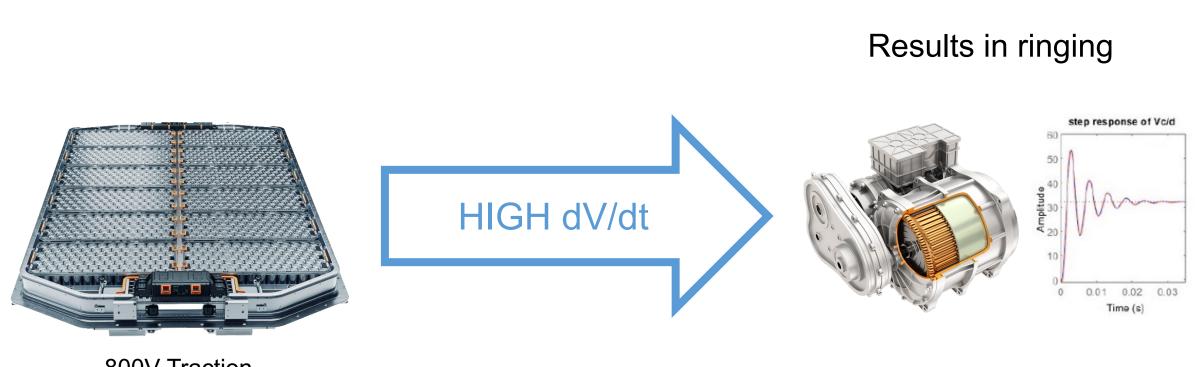

800V Traction Battery

Extra components


- Weight
- Cost
- Lifecycle
- Wasted Power
- Mechanical

Why precharge fails

- Heat
- Repeated cycling in a short period causes the precharge resistor to overheat
- Accidentally having a load on, then the precharge never completes and burns up the precharge resistor
- If not used correctly designed, it easily destroys the HV circuits due to in-rush currents

Capacitance	Battery Voltage	Resistor Value	Precharge time	Avg Power
4mF	800V	50 Ohm	1.0 sec	1280W
4mF	800V	100 Ohm	2.0 sec	640W
6mF	800V	50 Ohm	1.5 sec	1280W
6mF	800V	100 Ohm	3.0 sec	640W

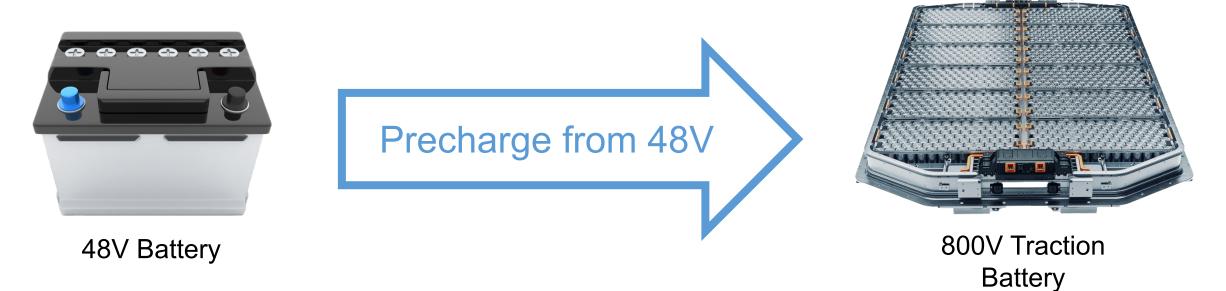12V Battery / Supercapacitor48V Battery / Supercapacitor




Regulation required


Regulator required in the series powertrain


Regulated Option	Advantage / Disadvantage
12V to 48V Conversion	High current levels with high losses
48V to 48V Conversion	Lowest current and highest efficiency
48V to 800V Conversion	Most difficult and expensive

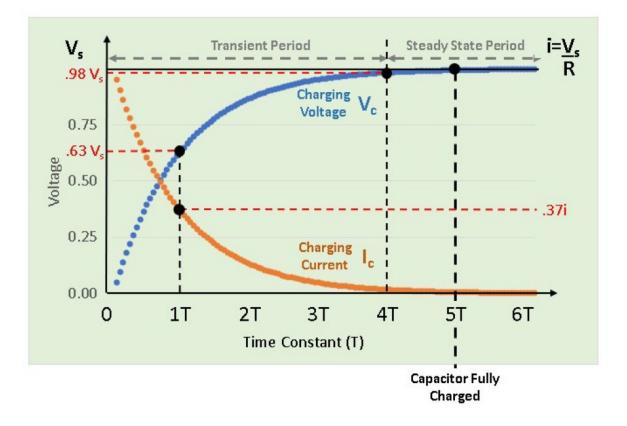Charge time inversely proportional to power level



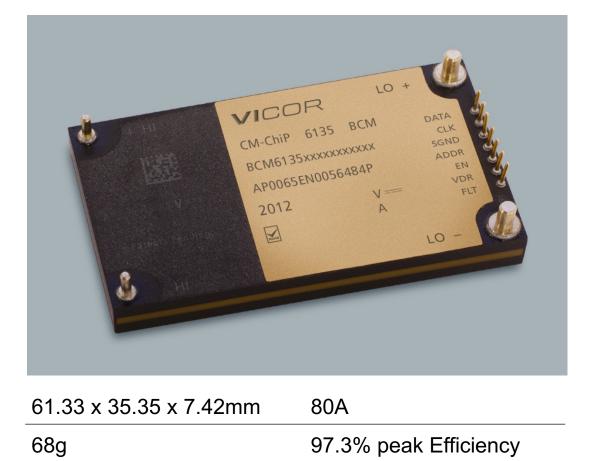
- Isolated
- Controllable $V_{\mbox{\scriptsize OUT}}$ on the low side
- Has PMBus[®] to monitor the voltage
 - Readout from PMBus
 - HV is on the other side of the contactor → very useful




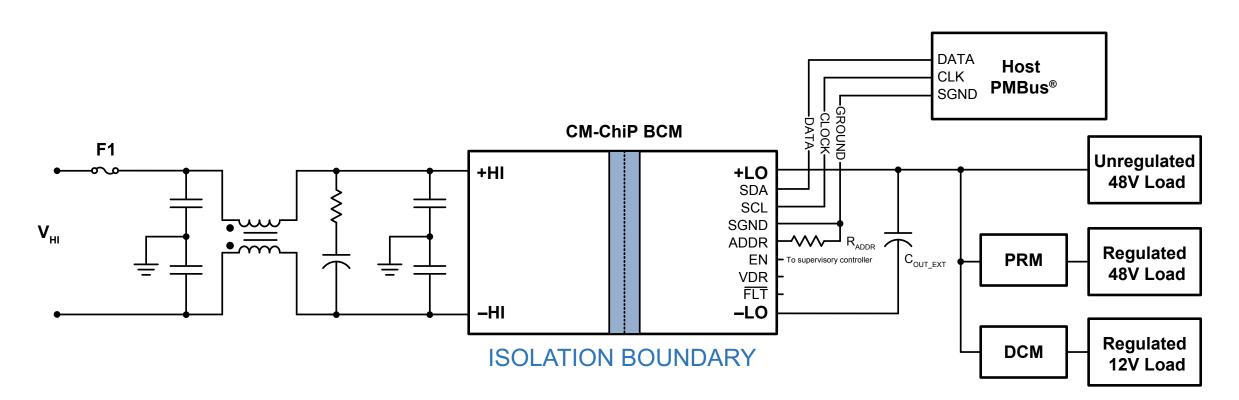


Need to control the ramp as C_{OUT} HI is limited to 0.39µF and the DC link cap is ~58µF and any input capacitance from loads

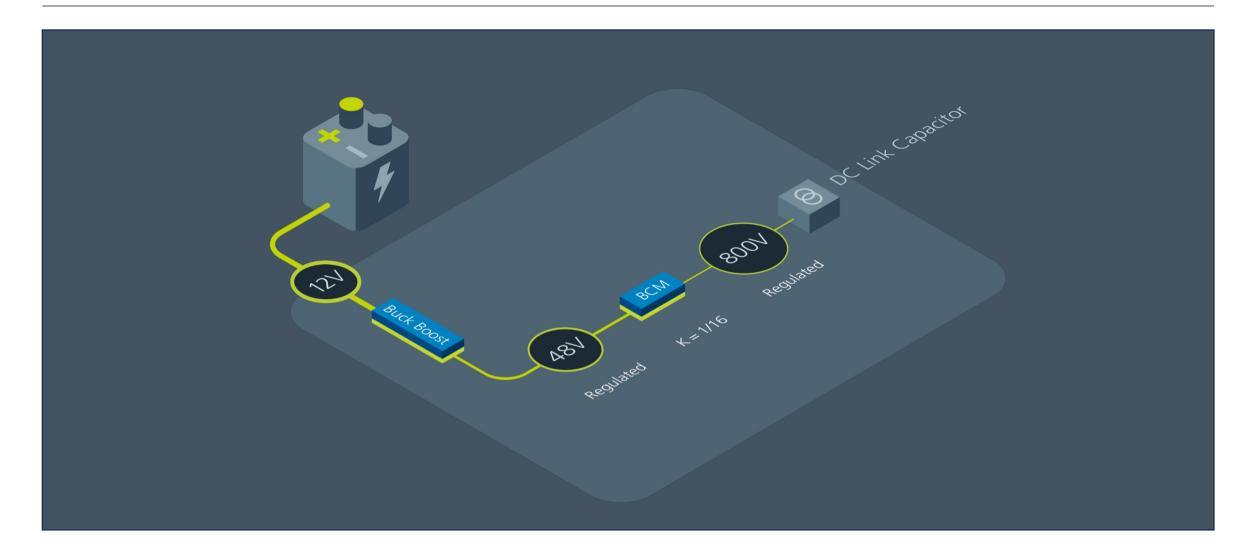
Using a 12V battery enables low-power regulated 48V bus at no cost




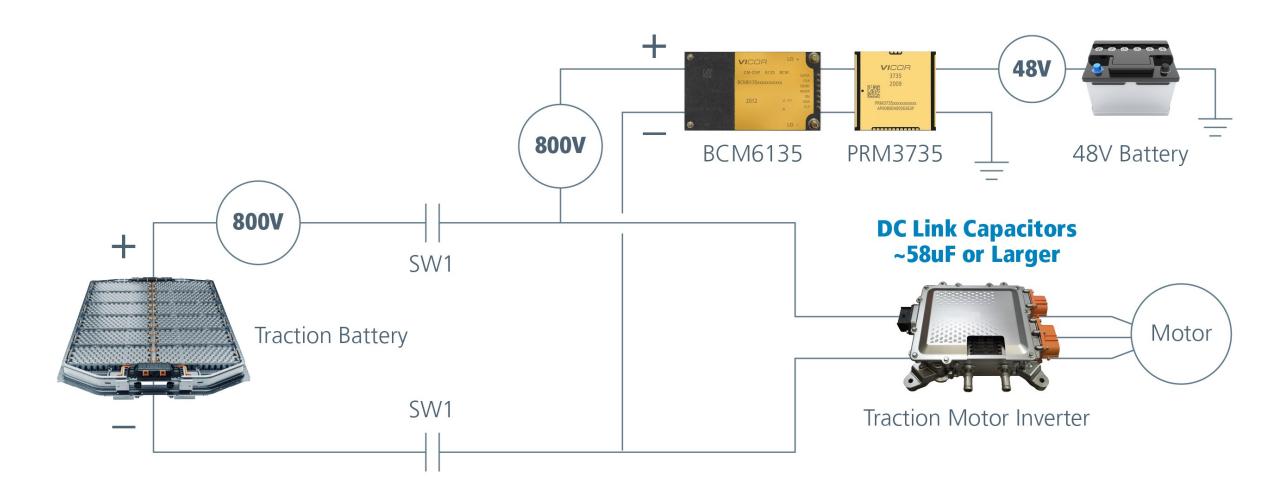

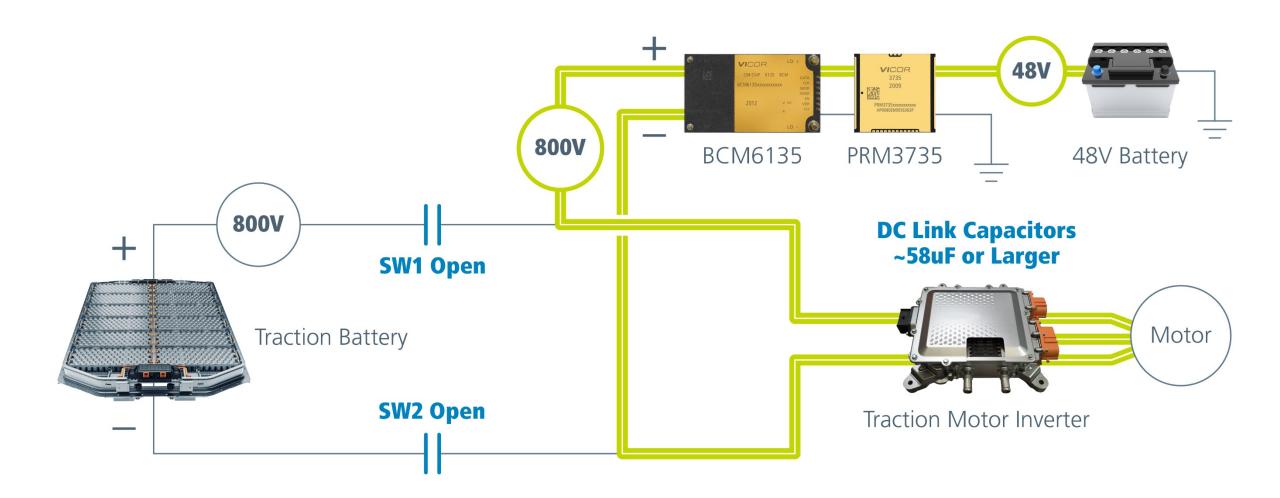

The Vicor Solution

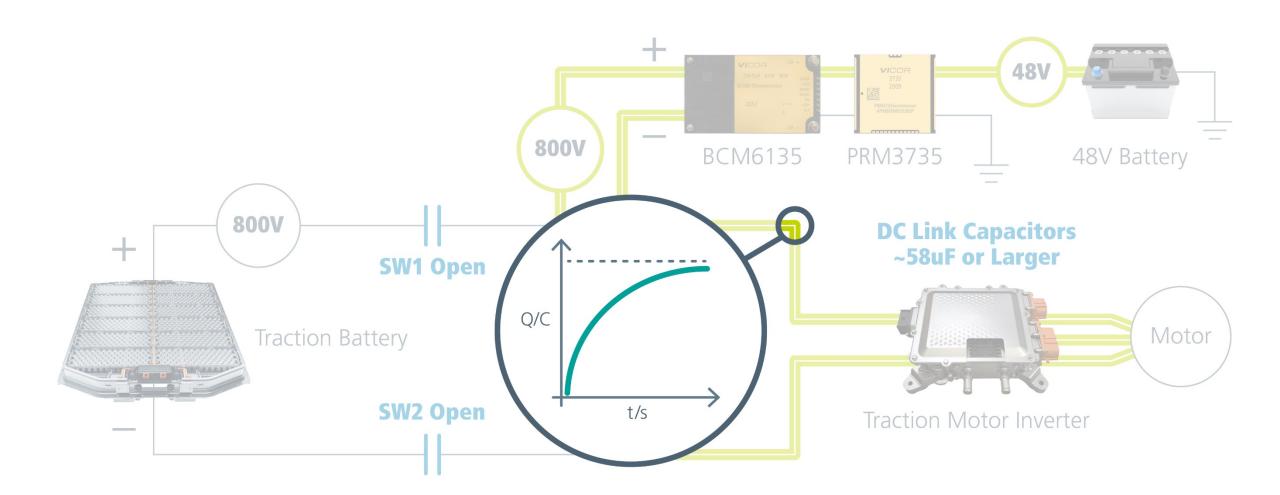


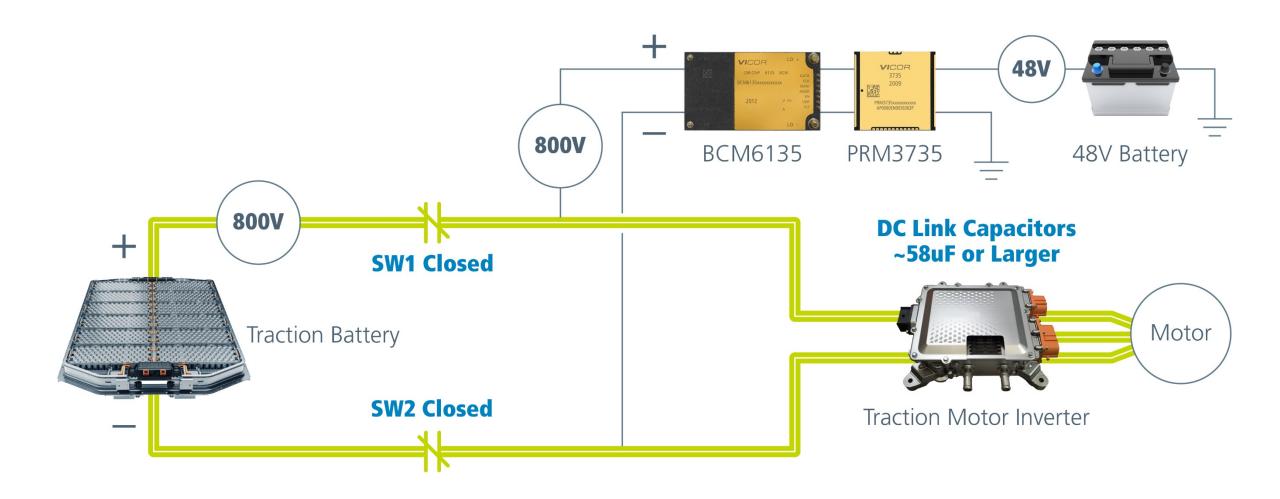

- Use a 48V source charging an 800V load with BCM6135 (K = 1/16)
- Use a buck-boost with current control capability
 - Set current to 4.9A
 - Alternative ramp-up voltage on the 48V side slowly
 - Maintain 5A or lower on high side

High side (800V)	Low side (400V)	
800V	48V	
5A	80A	

Charging the HV Bus from 48V Source

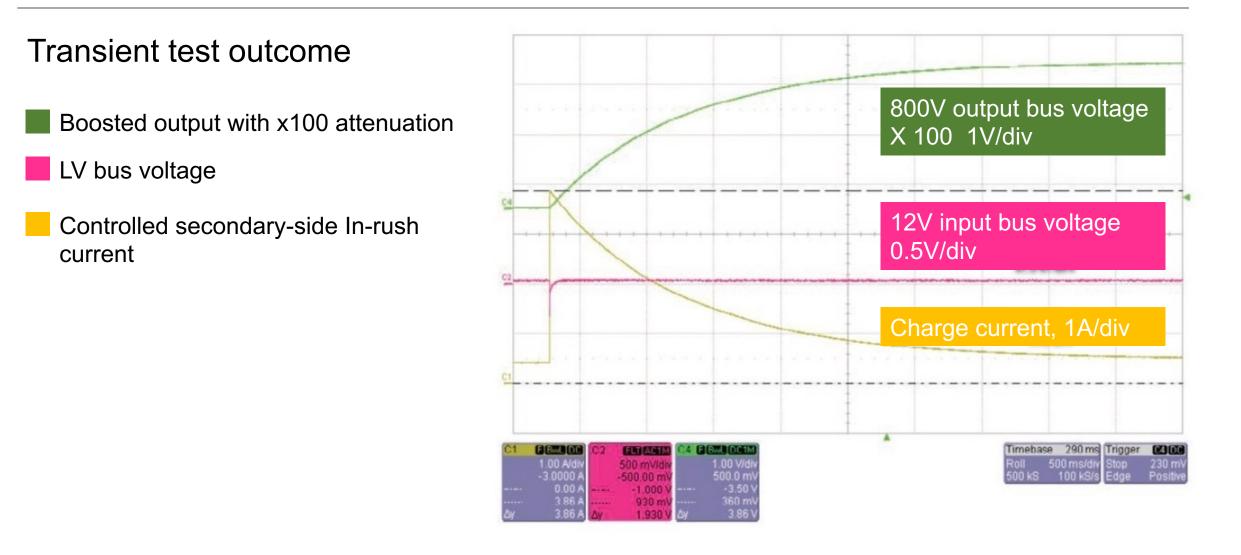

- Reuse existing hardware
- Cost savings
- Safer
- Compact in size

- High efficiency
- No series resistor
- Longer range
- Future proof
- Energy savings
- Safer to prevent overheating or fires
- Weight savings
- Faster
- Get a bonus 48V node





Thank you

Patrick Kowalyk, Automotive FAE Vicor Corporation 25 Frontage Rd, Andover, MA 01810, USA pkowalyk@vicorpower.com or 630-551-5502







Questions?

